

Handwritten Notes
On
Capacitor



LearningMantrasOfficial



LearningMantras


CAPACITOR

* c does not depend on Q & V .

The capacity of conductor to store charge on its shape & size.

* Dielectric strength of medium \rightarrow It is max electric field after which insulation of medium get punched. for air = $3 \times 10^6 \text{ V/m}$

solid conducting sphere: \rightarrow

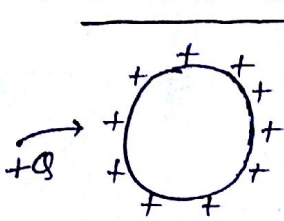

$$V_{\text{sphere}} = \left(\frac{1}{4\pi\epsilon_0} \right) \frac{Q}{R}$$

$$V_{\text{sphere}} - V_{\text{infinite}} = \Delta V = \frac{Q}{(4\pi\epsilon_0)R}$$

$$Q = (4\pi\epsilon_0 R) \Delta V$$

$$Q = C \Delta V$$

$$C = 4\pi\epsilon_0 R$$

* In conductor

$$Q(\uparrow) = V(\uparrow)$$

means, charge (Q) \propto pot. (V)

Unit \rightarrow MKS \rightarrow C/volt, Farad (F)
CGS \rightarrow stat farad
(1F = 9×10^{11} stat.F)

Imp #

C_{earth} = ?

* Theoretical value \rightarrow By considering it conductor of $6370(6400)$ km

$$C = 711 \mu\text{F}$$

* Practically \rightarrow earth can accept unlimited charge so its capacitance is infinite (∞)

* capacitance of any earth conductor is infinite.

EX \rightarrow



capacitance = c
take limited charge



capacitance = ∞
take unlimited charge

$$\left. \begin{matrix} \text{b/c } c = \frac{Q}{V} = \frac{Q}{0} = \infty \end{matrix} \right\}$$

potential energy stored in charge conductor \rightarrow
Some external work is done during charging of conductor which is stored in form of pot. energy.

$$U = \frac{1}{2} c V^2 = \frac{1}{2} QV = \frac{Q^2}{2C}$$

* p.e \oplus only in charge conductor but capacitance \oplus in charge or, uncharge.

Energy spend by Battery

$$\because \text{Emf} = V$$

$$1 \text{ charge} \rightarrow \text{Work} = V$$

$$Q \rightarrow \text{Work} = QV$$

$$\text{Work by battery} = \Delta U + \text{Heat}$$

$$QV = \left(\frac{1}{2}QV - 0\right) + \text{Heat}$$

$$\text{Heat} = \frac{1}{2}QV$$


EX → For a conductor

$$\text{If charge} = Q = PE = U$$

$$\text{then charge} = Q/2 = PE = ?$$

$$C = \text{const.}, U = \frac{Q^2}{2C} \propto Q^2, U' = \frac{U}{4}$$

** # Re-distribution of charge: →

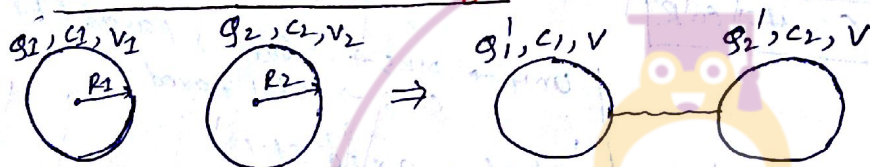

* $C_{\text{system}} = C_1 + C_2 + C$ ← It is capacitance of conductor wire it is negligible.

$$C_{\text{system}} = C_1 + C_2$$

* Total charge of system is re-distributed is ratio of capacitance.

$$Q \propto CV$$

$$Q \propto C \propto R$$

* $V_{\text{common}} = ?$

$$Q_1 + Q_2 = Q_1' + Q_2'$$

$$C_1V_1 + C_2V_2 = C_1V + C_2V$$

$$V_{\text{common}} = \frac{C_1V_1 + C_2V_2}{C_1 + C_2}$$

$$V_{\text{common}} = \frac{Q_1 + Q_2}{C_1 + C_2}$$

$$V_{\text{system}} = \frac{Q_{\text{system}}}{C_{\text{system}}}$$

* Energy loss (ΔU)

$$U_{\text{Initial}} = \frac{1}{2}C_1V_1^2 + \frac{1}{2}C_2V_2^2$$

$$U_{\text{Final}} = \frac{1}{2}C_1V^2 + \frac{1}{2}C_2V^2$$

$$U_{\text{Initial}} - U_{\text{Final}}$$


$$\Delta U = U_{\text{Final}} - U_{\text{Initial}}$$

$$\Delta U = \frac{C_1C_2}{2(C_1+C_2)} (V_1 - V_2)^2$$

NOTE → During charging half of energy spend for battery is stored in the form of P.E of conductor & remaining half wasted in form of Heat in connected wire.

Concept of capacitor : \rightarrow ^{AIR} Generally, capacitors are formed by using 2 conductors having equal & opposite charge on them. The advantage of using opp. charge is to confine all the electrical energy in certain volume so that it can be easily extracted when required.

Case I

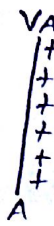

pot. of plate A

$$V_A' = V_A - V_B^- + V_B^+$$

$$\therefore |V_B^-| > |V_B^+| \quad \left(\text{Here } B^- \text{ more due to more impact of plate A} \right)$$

$$\Rightarrow V_A' < V_A$$

$$\therefore C = \frac{Q}{V(\downarrow)} = C(\uparrow)$$

Case II



$$V_A'' = V_A - V_B^-$$

$$V_A'' \ll V_A$$

$$\therefore C = \frac{Q}{V(\downarrow\downarrow)} = C(\uparrow\uparrow)$$

AIR

* \rightarrow When a neutral or, opp. charge conductor is placed near a charge conductor then charge of 1st conductor remains unchange while pot. change significantly. So capacitance \uparrow

Type of capacitor \rightarrow

iii \rightarrow Parallel Plate capacitor (PPC) \rightarrow

$$C = \frac{A\epsilon_0}{d}$$


liii \rightarrow Spherical capacitor \rightarrow

$$C = 4\pi\epsilon_0 \left(\frac{ab}{b-a} \right)$$

liiii \rightarrow Cylindrical capacitor \rightarrow

$$C = \frac{2\pi\epsilon_0 L}{\ln \frac{R_2}{R_1}}$$

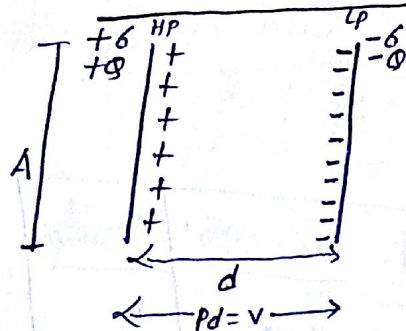iii \rightarrow parallel plate capacitor : \rightarrow



(a) \rightarrow Electric field (E) \rightarrow

$$\left[\begin{array}{l} E_{\text{inside}} = \frac{\sigma}{\epsilon_0 \epsilon_r} = \frac{V}{d} \quad (\text{uniform}) \\ E_{\text{outside}} = 0 \end{array} \right]$$

(b) \rightarrow Pot. energy (U) \rightarrow

$$U = \frac{1}{2} CV^2 = \frac{1}{2} QV = \frac{Q^2}{2C}$$

(c) \rightarrow Energy density / Electrostatic pressure (u) \rightarrow energy store in unit vol.

$$u = \frac{\text{Energy}}{\text{vol.}}$$

$$U = \frac{1}{2} \frac{\epsilon_0}{a} \left(\frac{V}{d} \right)^2 = \frac{1}{2} \epsilon_0 E^2$$

$$* U = \left\{ \frac{1}{2} \epsilon_0 \left(\frac{\sigma}{\epsilon_0} \right)^2 = \frac{\sigma^2}{2\epsilon_0} \right\}$$


1d) → Attraction force b/w // plate: →

$$= \frac{\sigma^2}{2\epsilon_0} \quad \left| \quad F = \left(\frac{\sigma^2}{2\epsilon_0} \right) A \right. *$$

$$= \left(\frac{\sigma^2}{2\epsilon_0} \right) A$$

1e) → capacitance (C) →

|Air| $C_{air} = \frac{\epsilon_0 A}{d}$


 $C_{med} = \frac{\epsilon_0 \epsilon_r A}{d}$


∴ $C_{med} = \epsilon_r C_{air}$
 ∴ $\epsilon_r > 1$
 ⇒ $C_{med} > C_{air}$

If $C_{air} = C_{med}$

$$\frac{\epsilon_0 A}{d_{air}} = \frac{\epsilon_0 \epsilon_r A}{d_{med}}$$


$$d_{air} = \frac{d_{med}}{\epsilon_r}$$

 $C_{partial} = \frac{\epsilon_0 A}{(d-t) + t/\epsilon_r}$


 $C = \frac{\epsilon_0 A}{(d-t_1-t_2) + \left(\frac{t_1}{\epsilon_{r1}} + \frac{t_2}{\epsilon_{r2}} \right)}$

* capacitance is independent of position of slab with respect to plate

Variation in charge PPC →

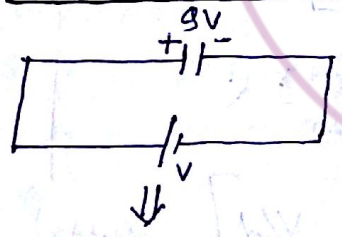

$V_c = \text{const}$
(battery connected)

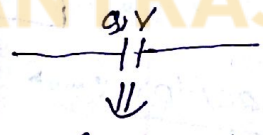

$Q_c = \text{const}$
battery disconnected

Case-I → Battery^{dis}connected ($Q_c = \text{const}$): →

Variation	$C = \frac{\epsilon_0 \epsilon_r A}{d}$	$V_c = \frac{Q}{C}$	Q $Q_c = \text{const}$	$E = \frac{Q}{A \epsilon_0 \epsilon_r}$	$V_c \propto \frac{Q}{\epsilon_r C}$
$\epsilon_r (\uparrow)$	\uparrow	\downarrow	\leftrightarrow	\downarrow	\downarrow
$A (\uparrow)$	\uparrow	\downarrow	\leftrightarrow	\downarrow	\downarrow
$d (\uparrow)$	\downarrow	\uparrow	\leftrightarrow	\leftrightarrow	\uparrow


Case II \Rightarrow Battery connected ($V_c = \text{const}$)

Variation	$C = \frac{\epsilon_0 \epsilon_r A}{d}$	$V_c = \text{const}$	$Q \propto C$ $Q_c = CV$	$E = \frac{V}{d}$	$U_c = \frac{1}{2} CV^2$
$\epsilon_r \uparrow$	\uparrow	\leftrightarrow	\uparrow	\leftrightarrow	\uparrow
$A \uparrow$	\uparrow	\leftrightarrow	\uparrow	\leftrightarrow	\uparrow
$d \uparrow$	\downarrow	\leftrightarrow	\downarrow	\downarrow	\uparrow


* If nothing is given in question then consider battery disconnected.

Grouping of capacitor \Rightarrow

Series

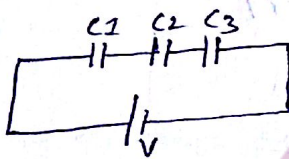

parallel

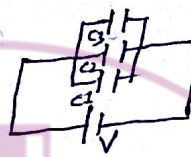

$\rightarrow Q = \text{same}$

$$\rightarrow \frac{1}{C_{\text{net}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\rightarrow C_{\text{net}} = \frac{C_1 \times C_2}{C_1 + C_2}$$

\rightarrow voltage distribution

$$V \propto \frac{1}{C}$$

$$V_1 : V_2 : V_3 = \frac{1}{C_1} : \frac{1}{C_2} : \frac{1}{C_3}$$

$\rightarrow V = \text{same}$

$$\rightarrow C_{\text{net}} = C_1 + C_2 + C_3$$

\rightarrow charge distribution

$$Q = CV$$


$$Q \propto C$$

$$Q_1 : Q_2 : Q_3 = C_1 : C_2 : C_3$$

Distribution in PPC by dielectric medium \rightarrow


| Air | PPC | $C = \frac{\epsilon_0 A}{d}$

|a| \rightarrow Division in distance \rightarrow

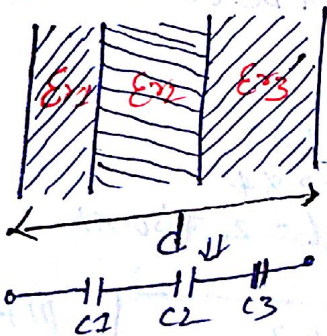

[Each section is capacitor & all capacitor are in series]

EX →

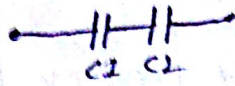


$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$C_{eq} = \frac{2\epsilon_1 \epsilon_2}{\epsilon_1 + \epsilon_2}$$



$$C_{eq} = \frac{\epsilon_0 A}{(d - t_1 + t_2) + \left(\frac{t_1 + t_2}{\frac{\epsilon_1}{\epsilon_2}}\right)}$$

* Equivalent dielectric const $(\epsilon_r)_{eq} = \frac{2\epsilon_1 \epsilon_2}{\epsilon_1 + \epsilon_2}$

1b) → Division in Area: →

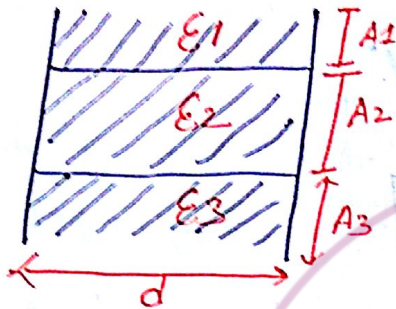

[Each section is a capacitor and all capacitor are in ||.]

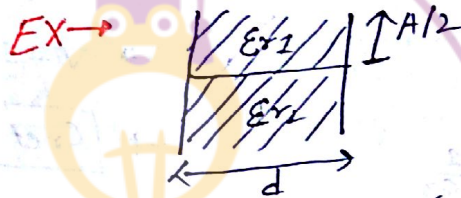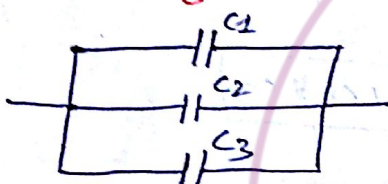

$$C_{eq} = C_1 + C_2 = \left(\frac{\epsilon_1 + \epsilon_2}{2}\right) C$$

$$(\epsilon_r)_{eq} = \frac{\epsilon_1 + \epsilon_2}{2}$$

*

$\frac{x \& y}{A \cdot M} \Rightarrow \frac{x+y}{2}$

$$A \cdot M \Rightarrow \frac{x+y}{2}$$

LEARNING MANTRAS

$$G \cdot M = \sqrt{xy}, \quad H \cdot M = \frac{2xy}{x+y}$$

Multiple capacitor →

→ * Given plate arrangement converted into equivalent circuit using point potential method.

ii) → No. of all plate is done

iii) → For making capacitor plate should be conductive there pot. should be diff.

EX →


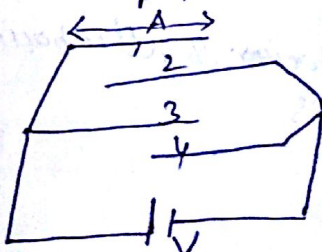


plate = 4

conductor = 2 → 1 & 3, 2 & 4

separate potential = 2 = point

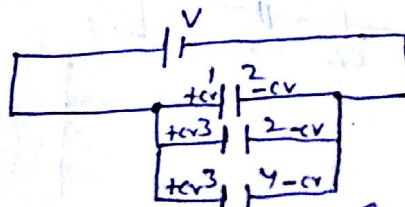

iii) → charge on each plate

$$Q_1 = +CV$$

$$Q_2 = -CV - CV = -2CV$$

$$Q_3 = +CV + CV = +2CV$$

$$Q_4 = -C$$

$$ii) \rightarrow C_{eq} = 3C = 3\left(\frac{\epsilon_0 A}{d}\right)$$

* $\frac{3e}{\rightarrow}$ In case of n-parallel plate, if alternate plate are connected with each other then max (n-1) capacitor are there in parallel grouping so, $C_{max} = (n-1)C$

Spherical capacitor \Rightarrow

Case I \rightarrow If ^{inner} sphere is charged & outer is earthed \rightarrow



$$V_{small} = \frac{kq}{r} - \frac{kq}{R}$$

$$V_{big} = \frac{kq}{R} - \frac{kq}{R} = 0$$

pot. difference

$$V = kq \left(\frac{1}{r} - \frac{1}{R} \right), \quad V = \frac{kq}{4\pi\epsilon_0} \left(\frac{R-r}{Rr} \right)$$

$$\frac{q}{V} = \frac{4\pi\epsilon_0 Rr}{R-r}$$

$$C_1 = \frac{4\pi\epsilon_0 Rr}{R-r}$$

* If $r = \text{fixed}$ $R = \uparrow$ then capacitance = ?

$$C = \frac{4\pi\epsilon_0 r}{1 - \frac{r}{R}} \quad (\text{divided by } R)$$

$C = \downarrow$ bcoz $\frac{r}{R} \downarrow$ so, $1 - \frac{r}{R} \uparrow$ something by $\frac{1}{\text{constant}} (\downarrow)$


* If $r = \text{fixed}$, $R \downarrow$ then capacitance $\rightarrow \uparrow$

* If $R = \infty$ then capacitance ?

$$C = \frac{4\pi\epsilon_0 \epsilon_r r}{1 - \frac{r}{R}} \quad (C = 4\pi\epsilon_0 \epsilon_r r)$$

Each individual conductor is also a capacitor considering that its other conductor is at infinite.

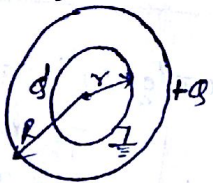Case II \rightarrow If outer sphere is charged & inner is earthed.



AS inner sphere is earthed the some charge q' is shifted from earth to this sphere for making its pot zero.

$$V_{big} = \frac{kq}{R} + \frac{kq'}{R}$$

$$V_{small} = 0$$

$$\therefore \text{P.D. } V = \frac{kq}{R} + \frac{k}{R} \left(-\frac{r}{R} q \right)$$

$$V = \frac{kq}{R} \left(1 - \frac{r}{R} \right)$$

$$V = \frac{q}{4\pi\epsilon_0 \epsilon_r R} \left(\frac{R-r}{R} \right)$$

$$C_{II} = 4\pi\epsilon_0 \epsilon_r R \left(\frac{R}{R-r} \right)$$


$$C_{II} = \frac{4\pi\epsilon_0 \epsilon_r Rr}{R-r} + 4\pi\epsilon_0 \epsilon_r R$$

$$C_{II} = C_I + 4\pi\epsilon_0 \epsilon_r R$$

$$C_{II} > C_I$$

* If nothing is given in question then we use case I

charging & discharging of capacitor →

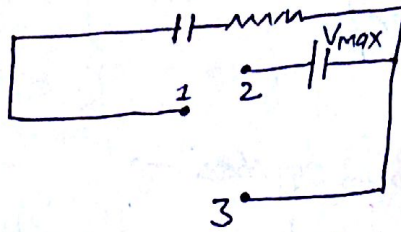

case I → charging →

(1-2)

$t = 0$	$t = \uparrow$	$t = \infty$ (full charging)
$V_c = 0$	$V_c = \uparrow$	$V_c = V_{max}$ (max)
$Q_c = 0$	$Q_c = \uparrow$	$Q_c = CV_{max}$ (max)
$U_c = 0$	$U_c = \uparrow$	$U_c = \frac{1}{2} CV_{max}^2$ (max)
$I_{ckt} = \frac{V_{max}}{R}$ (max)	$I_{ckt} \downarrow$	$I_{ckt} = 0$


* Here, R is used to safe the capacitor from starting excess current.

By KVL


$$V_c = V_{max} (1 - e^{-t/RC})$$

$$I_{ckt} = I_{max} e^{-t/RC}$$

Graph b/w V_c & t

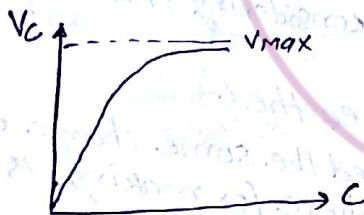

Graph b/w I_{ckt} & t

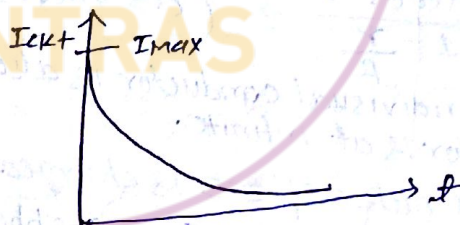

$$e = 2.73$$

$$\frac{1}{e} = 0.37$$

$$e^0 = 1$$

$$e^\infty = \infty$$

$$e^{-\infty} = 0$$

$$\log_{10} 2 = 0.301$$

$$\log_{10} 3 = 0.473$$

$$\log_{10} 5 = 0.699$$

$$\log_e x = 2.303 \log_{10} x$$

$$\log_e 2 = 2.303 \log_{10} 2 = 2.303 \times 0.301 = 0.693$$

$$\log_{10} e = 0.434, \log_{10} 10 = 1$$

Time cost (τ) → It is time in which approx 63% working take place.

$$V_c = V_{max} (1 - e^{-t/RC})$$

* If $t = RC$

$$V_c = V_{max} (1 - e^{-1})$$

$$V_c = 0.63 V_{max}$$

$$\tau = RC$$

* +

$$t = 5\tau = 99.3\%$$

$$t = \tau = 63\%$$

* Heat produced = $\frac{1}{2} CV^2$ [not depend on resistance]

* If $R \uparrow \Rightarrow$ Heat \leftrightarrow
 timing \uparrow
 $I_{ckt} \downarrow$


* If $R \downarrow \Rightarrow$ Heat \leftrightarrow
 timing \downarrow
 $I_{ckt} \uparrow$

* Time for 99% charging $\rightarrow 0.921 RC$
 Trick * $1\tau = 200.1 \mu sec$
 $5\tau = 2000.1 \mu sec$
 $t = 5\tau = 99.9\%$ Work done so $t =$ less than $1000 \mu sec$.
 * time for 50% charging $\rightarrow t = 200 \times 10^{-6} \times 0.693 = t = 138.6 \mu sec$.

case II \Rightarrow Discharging \rightarrow


$t = 0$	$t = \uparrow$	$t = \infty$ (Full discharge)
$V_c = V_{max}$	$V_c = \downarrow$	$V_c = 0$
$q_c = q_{max}$	$q_c = \downarrow$	$q_c = 0$
$U_c = \frac{1}{2} CV^2_{max}$	$U_c = \downarrow$	$U_c = 0$
$I_{ckt} = \frac{V_{max}}{R}$	$I_{ckt} = \downarrow$	$I_{ckt} = 0$

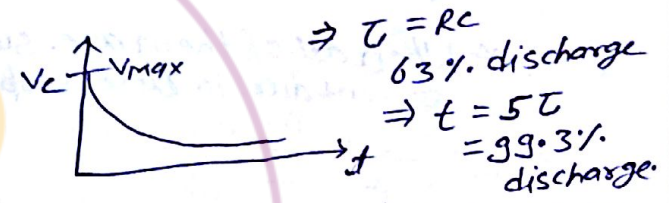$\therefore V_c = V_{max} e^{-t/RC}$
 $I_{ckt} = -I_{max} e^{-t/RC}$



Trick * $\tau = 1 sec$ \Rightarrow 63% discharge ho jayega, so 50% discharge less than 1 sec.

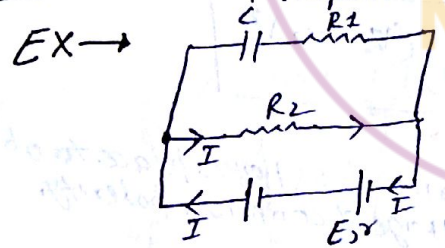RC CKT \rightarrow In steady state condⁿ capacitor are fully charge so current in capacitor branched is zero.



In stable condⁿ find charge on capacitor

$I = \frac{E}{R_2 + R_1}$
 $\therefore V_{R_2} = I \times R_2 = \frac{R_2}{R_2 + R_1} E$

$\therefore V_{R_1} = \text{const} \times R_1 = 0 \times R_1 = 0$
 $V_{c1} = V_{R_2} = \frac{R_2}{R_2 + R_1} E$
 $Q = CV_c = \frac{R_2}{R_2 + R_1} CE$


* If $R_2 \uparrow \Rightarrow Q = ?$

$Q = \frac{R_2}{R_2 + R_1} CE$


Trick $\left[\frac{R_2}{R_2 + R_1} \text{ ratio } \text{का } +1 = \text{का } , \text{ something upon } \text{का } \text{ (का } \text{का } \right]$

NOTE \rightarrow * At $(t=0)$, $I = I_{max}$ 'c' is like short ckt.
 * At $(t=\infty)$, $I = 0$ 'c' is like open ckt.

To connect two charge PPC →

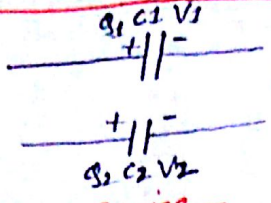


Case-I → Series -

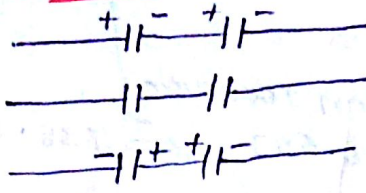

!! * No close loop so no charge flow so no change in detail of capacitor.


III
**
EX →

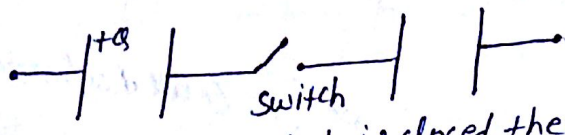

After switch on after long time what will charge on uncharged capacitor.

Ans → When switch is closed then no charge flow in uncharged capacitor due to no close loop.

III
EX →

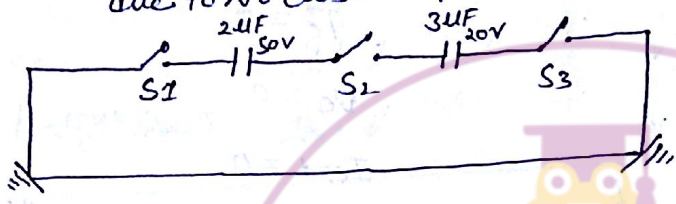


* If any one or two switch are made on then there is no close loop no charge, no current flow so, the details of charge & voltage remains same.

* When all of them are switch are made then there is charge in charge current due to close loop is formed.

Case II → parallel -

1a → To connect same polarity ends →

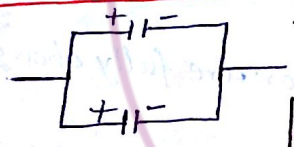


* If voltage are different then charge sharing take place to obtain same voltage.

$$V_{\text{common}} = \frac{V_1 C_1 + V_2 C_2}{C_1 + C_2}$$

$$\Delta U = \frac{C_1 C_2}{2(C_1 C_2)} (V_1 - V_2)^2$$

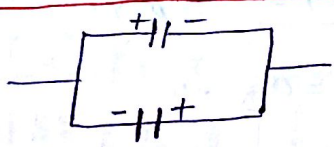1b → To connect opposite polarity plate →



* charge sharing does take place to obtain common voltage & common polarity.

$$V_2 \rightarrow -V_2$$

$$V_{\text{common}} = \frac{C_1 V_1 - C_2 V_2}{C_1 + C_2}$$

$$\Delta U = \frac{C_1 C_2}{2(C_1 C_2)} (V_1 + V_2)^2$$


(plus)

* Nothing is said in q. then we assume same polarity.

* NOTE → If $C_2 = xC$, the $V_1 = C$, $V_2 = V/xC$ b/c $q = \text{constant}$ $q = CV$
 $V \propto \frac{1}{C}$

Different cases of capacitor

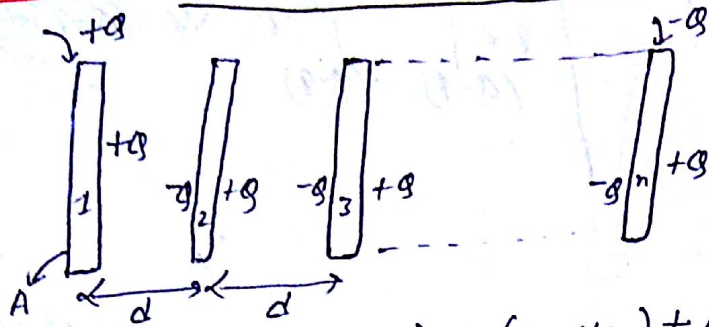Case-I \Rightarrow 'n' no. of plates are placed: -



$$V_1 - V_n = (V_1 - V_2) + (V_2 - V_3) + (V_3 - V_4) + \dots + (V_{n-1} - V_n)$$



$$\Delta V = \frac{Qd}{A\epsilon_0} + \frac{Qd}{A\epsilon_0} + \dots + \frac{Qd}{A\epsilon_0}$$

$$\Delta V = \frac{Qd(n-1)}{A\epsilon_0}$$

$$Q = \left[\frac{A\epsilon_0}{(n-1)d} \right]$$

$$* C = \frac{A\epsilon_0}{(n-1)d}$$

Case-II \Rightarrow

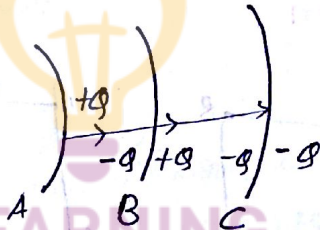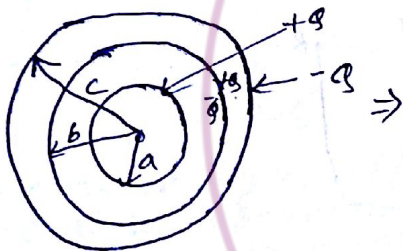

$$V_A = \frac{kQ}{a} - \frac{kQ}{c}$$


$$V_C = \frac{kQ}{c} - \frac{kQ}{c} = 0$$

$$\Delta V = V_A - V_C = kQ \left[\frac{c-a}{ac} \right]$$

$$Q = \frac{(4\pi\epsilon_0)ac \Delta V}{(c-a)}$$

$$* C = \frac{(4\pi\epsilon_0)ac}{c-a}$$

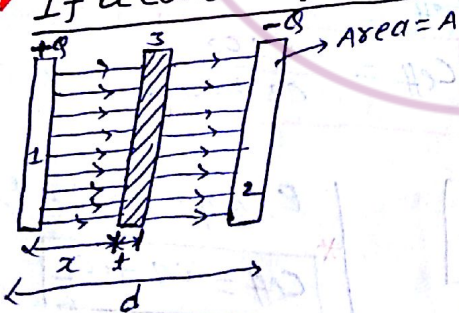Case-III \Rightarrow If a conducting slab with thickness 't' is introduced. \rightarrow




$$V_1 - V_2 = (V_1 - V_3) + (V_3 - V_2)$$

$$= \frac{Qx}{A\epsilon_0} + \frac{Q(d-t-x)}{A\epsilon_0}$$

$$\Delta V = \frac{Q(d-t)}{A\epsilon_0}$$




$$* C = \frac{A\epsilon_0}{d-t}$$

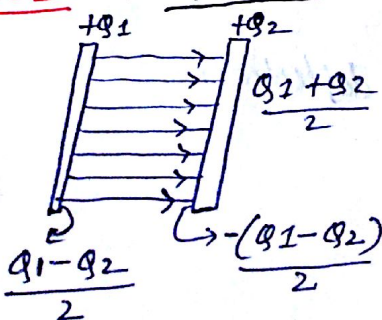Case-IV \Rightarrow Actual charge on capacitor \rightarrow




$$* \text{charge on capacitor} = \frac{Q_1 - Q_2}{2}$$

Battery & capacitor →

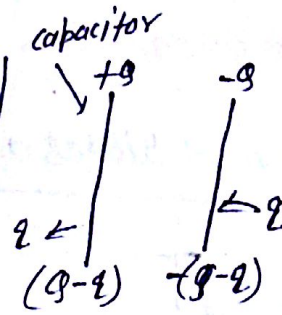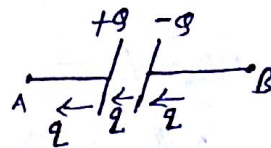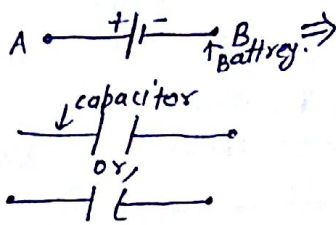

$$V_i = \frac{Qd}{A\epsilon_0}$$

$$V_f = \frac{(Q-Q)d}{A\epsilon_0}$$

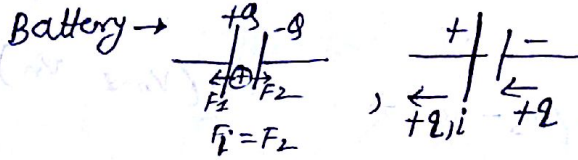


* ⊕ve charge will leave from ⊕ve terminal & must enter the ⊖ve terminal of the battery.

* Inside the battery charge is taken from lower pot. plate to higher pot. plate with the help of battery mechanism.

• Work done by battery = charge flow (Q) × pot difference b/w terminal. (Emf of battery)

Series & parallel combination


Series combination

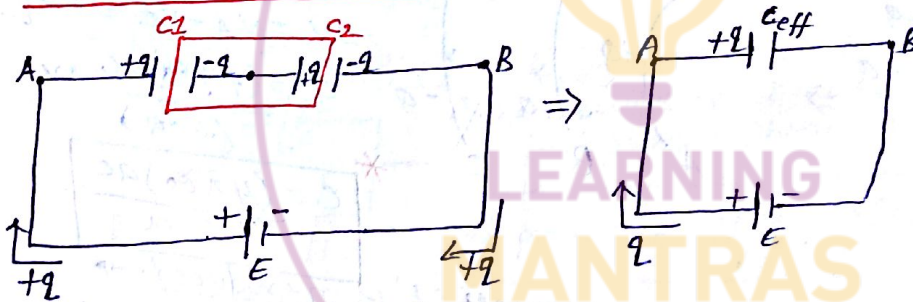

$$V_A - V_B = \frac{Q}{C_1} + \frac{Q}{C_2} = \frac{Q}{C_{eff}} = E \quad , \quad \frac{1}{C_{eff}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$* \quad C_{eff} = \frac{C_1 C_2}{C_1 + C_2}$$

Parallel combination

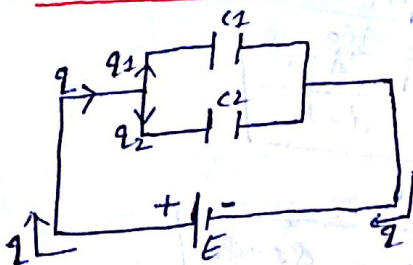

$$* \quad \frac{Q_1}{Q_2} = \frac{C_1}{C_2}$$

$$Q = Q_1 + Q_2$$

$$E \times C_{eff} = E \times C_1 + E \times C_2$$

$$* \quad C_{eff} = C_1 + C_2$$



NOTE Wheatstone Bridge

When galvanometer should null (zero) deflection

$$\left. \begin{aligned} V_A - V_B &= +i_1 R_1 \\ V_A - V_D &= +i_2 R_2 \end{aligned} \right\} V_B - V_D$$

$$i_1 R_1 = R_2 i_2 \text{ --- (1) } , \quad i_3 R_3 = i_2 R_4 \text{ --- (2)}$$


$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

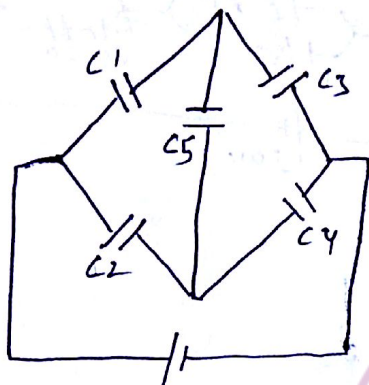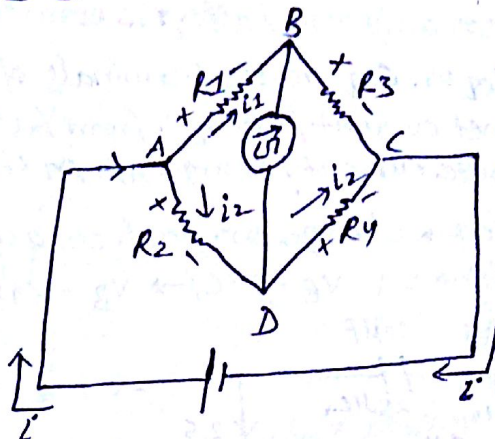


$$\frac{C_1}{C_2} = \frac{C_3}{C_4}$$

Balanced Wheatstone Bridge


Rules for Breaking or, folding of CKT.

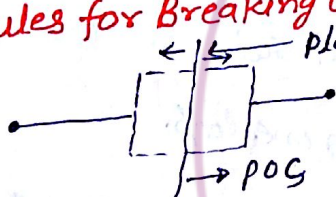

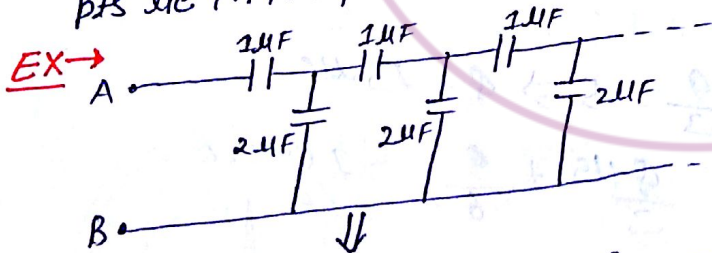- * We can join any no. of points which are laying on plane of symmetry. They all are at same potential.
- * We can break a point in CKT in any no. of points if after breaking all the pts lie in the plane of symmetry.


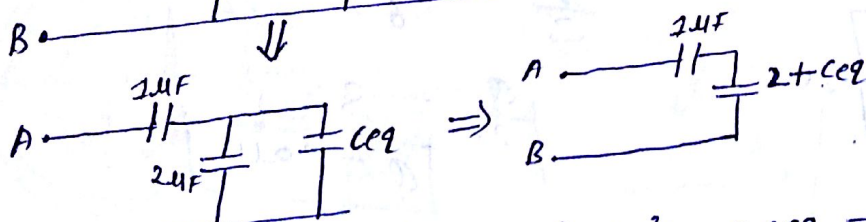
$$C_{eq} = \frac{-2 \pm \sqrt{4+8}}{2} = (-1 + \sqrt{3}) \mu F$$



$$\frac{1}{C_{eq}} = \frac{1}{2+C_{eq}} + \frac{1}{1}$$

$$C_{eq} = \frac{1 \times (2+C_{eq})}{1+2+C_{eq}}$$

$$C_{eq}^2 = 3C_{eq} = C_{eq} + 2$$

$$C_{eq}^2 - C_{eq} - 2 = 0$$


General ckt solving -

Case-I \Rightarrow When only one battery is connected -

- iii \rightarrow Find R_{eq} or, C_{eq} across terminals of battery.
- liii \rightarrow Find net current/charge from battery as $i_{net} = \frac{V}{R_{eq}}$ or, $Q_{total} = C_{eq} \times V$
- liiii \rightarrow Distribute current/charge A/C in the ckt.

EX \rightarrow Find \rightarrow |a| \rightarrow charge on each capacitor

|b| \rightarrow $V_A - V_B = ?$ |c| \rightarrow $V_B - V_D = ?$

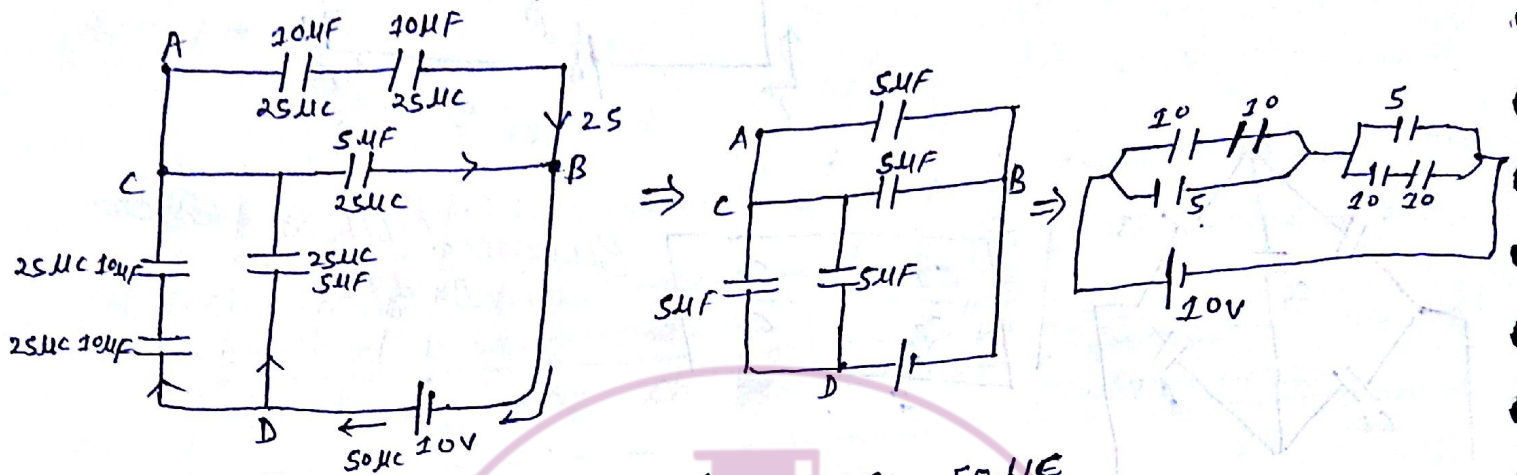

|a| $\rightarrow C_{eq} = 5\mu F$, $Q_{total} = 10 \times 5 = 50\mu C$


|b| $\rightarrow V_A - V_B = \frac{+25\mu C}{5\mu F} = +5V$

|c| $\rightarrow V_B - V_D = -10V$

Case-II \Rightarrow When more than one battery are connected -

- \rightarrow Apply loop rule (KVL) in each loop of ckt.
- \rightarrow Only one current/charge will exist along one loop.

EX \rightarrow

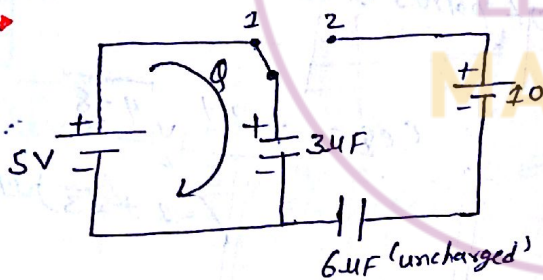

Initially switch was at position 1. Find final charge on capacitor when switch is thrown to position 2.


$$\frac{Q}{3} = 5 \Rightarrow Q = 15\mu C$$

$$\frac{Q+15}{3} + \frac{Q}{6} - 10 = 0$$

$$\frac{Q}{2} = 5$$

$$Q = 10\mu F$$

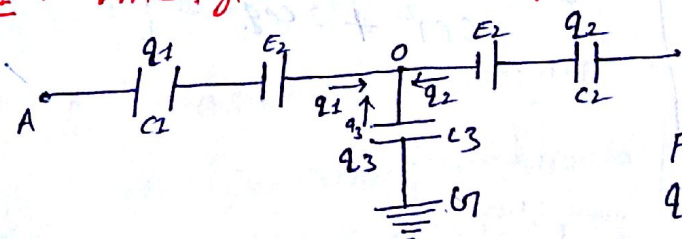Case-III \Rightarrow When given ckt is an open ckt.



Given $\Rightarrow V_A, V_B, C_1, C_2, C_3, E_1, E_2$

From KCL

$$q_1 + q_2 + q_3 = 0 \quad \text{--- (1)}$$

$$V_A - V_0 = \frac{q_1}{C_1} - E_1 \quad \text{--- (2)}$$



$$V_A - V_0 = \frac{+q_2}{C_2} + E_2 \quad \text{--- (3)}$$

$$V_{in} - V_0 = \frac{q_3}{C_3} \quad (4)$$

From (1) (2) (3) (4) $V = ?$

$q_1 = ? , q_2 = ? , q_3 = ?$

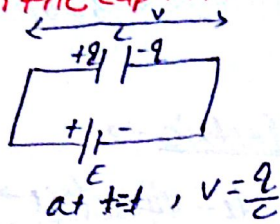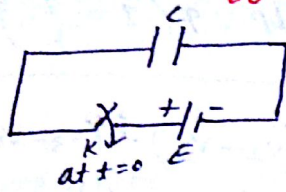*** # Potential energy stored in the capacitor :-



In next 'dt' time battery delivers dq charge to the capacitor
dW on capacitor

$$dW_{cap} = dU_{cap} = dq \cdot V$$

$$\int dU_{cap} = \int_0^Q \frac{q}{C} dq$$

$$* U_{cap} = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} CE^2 = \frac{1}{2} QE$$

Total Work done by battery.

$$* W_{batt} = QE = 2 U_{cap}$$

* Heat generated = H = $W_{battery} - \uparrow$ in PE of capacitor.

AIR

NOTE


→ Energy density / Electrostatic pressure (U) →



$$\vec{E} = \frac{Q}{A\epsilon_0}$$

$$U = \frac{1}{2} \frac{Q^2}{C} , U = \frac{Q^2 d}{2A\epsilon_0}$$
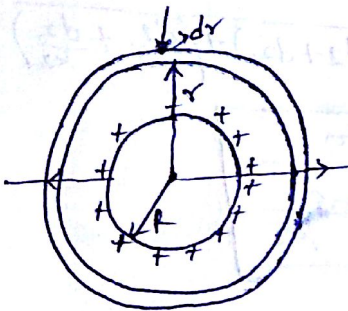
$$* U = \frac{U}{Ad} = \frac{Q^2}{2A^2\epsilon_0 d} = \frac{1}{2} \epsilon_0 E^2$$



$$C = 4\pi\epsilon_0 R$$

$$U = \frac{Q^2}{2C} = \frac{Q^2}{8\pi\epsilon_0 R}$$

$$* U_{self} = \frac{Q^2}{2C} = \frac{Q^2}{8\pi\epsilon_0 R}$$

For linear isotropic dielectrics →

$$\vec{E}_{net} = \vec{E}_{ext} + \vec{E}_{in}$$

$$|\vec{E}_{net}| = |\vec{E}_{ext}| - |\vec{E}_{in}|$$

$$* |\vec{E}_{net}| = \frac{|\vec{E}_{ext}|}{k}$$

dielectric const.

$$* \vec{E}_{in} = |\vec{E}_{ext}| - |\vec{E}_{net}|$$

$$* |\vec{E}_{in}| = |\vec{E}_{ext}| \left(1 - \frac{1}{k}\right)$$


For conductor

$$* k = \infty$$

$$* 1 \leq k \leq \infty$$

$$* k = 1 \rightarrow \text{For vacuum}$$

NOTE →

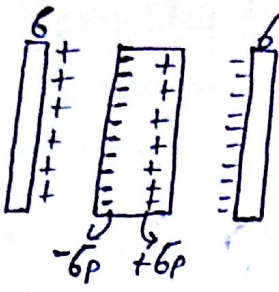

$$E_{\text{initially}} = \frac{\sigma}{\epsilon_0}$$


$$E_{\text{initially}} = \frac{\sigma}{K\epsilon_0}$$

$$\sigma - \sigma_p = \frac{\sigma}{K\epsilon_0}$$

$$\sigma_p = \sigma \left(1 - \frac{1}{K}\right)$$

$$Q_p = Q \left(1 - \frac{1}{K}\right)$$

Case IV → capacitor with dielectric →

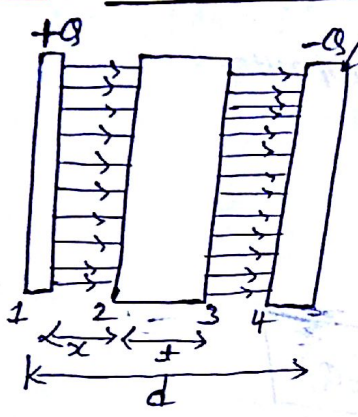

$$V_2 - V_4 = (V_1 - V_2) + (V_2 - V_3) + (V_3 - V_4)$$

$$\Delta V = \frac{Qx}{A\epsilon_0} + \frac{Qt}{KA\epsilon_0} + \frac{Q(d-x-t)}{A\epsilon_0}$$

$$C = \frac{A\epsilon_0}{d - t + \frac{t}{K}}$$

NOTE →


iii → If 'n' no. of plates with $(t_1, K_1), (t_2, K_2), (t_3, K_3), \dots, (t_n, K_n)$ are introduced,

$$C = \frac{A\epsilon_0}{d - (t_1 + t_2 + \dots + t_n) + \left(\frac{t_1}{K_1} + \frac{t_2}{K_2} + \dots + \frac{t_n}{K_n}\right)}$$

ii → If a conducting slab with thickness 't' is introduced,

$$C = \frac{A\epsilon_0}{d - t}$$

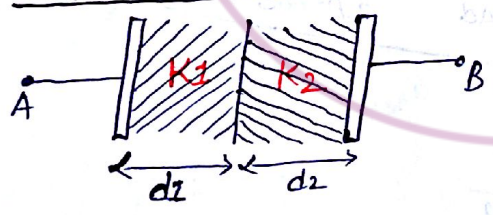Case V → capacitor filled with different dielectrics →




$$C = \frac{A\epsilon_0}{(d_1 + d_2) - (d_1 + d_2) + \left(\frac{d_1}{K_1} + \frac{d_2}{K_2}\right)}$$

$$C = \frac{A\epsilon_0}{\frac{d_1}{K_1} + \frac{d_2}{K_2}}$$

$$C_1 = \frac{K_1 A \epsilon_0}{d_1}$$

$$C_2 = \frac{K_2 A \epsilon_0}{d_2}$$

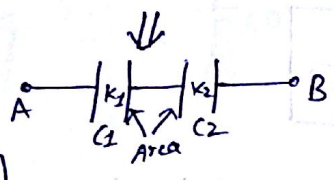

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

Case VI → Dielectric const is varying →

$$K = K_0 \left(1 + \frac{x}{L}\right)$$


$$dC = \frac{(L dx) \epsilon_0 K}{d}$$

$$K = K_0 \left(1 + \frac{x}{d}\right)$$

$$dC = \frac{L A K \epsilon_0 \left(1 + \frac{x}{d}\right)}{dx}$$

$$\int dx = \int \frac{K_0 \epsilon_0 L}{d} \left(1 + \frac{x}{L}\right) \cdot dx \quad \therefore \frac{1}{C_{eq}} = \int \frac{1}{dC} = \int \frac{dx}{\left(1 + \frac{x}{d}\right)} \times \frac{1}{L A K_0 \epsilon_0}$$

Ex 3

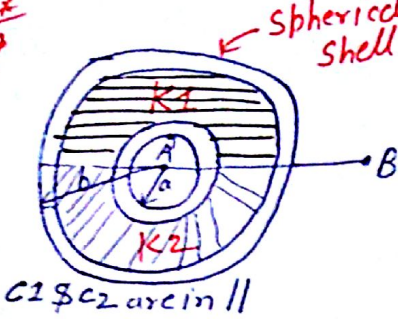

$$C_1 = \frac{2\pi\epsilon_0 abk_1}{b-a}$$

$$C_2 = \frac{2\pi\epsilon_0 abk_2}{b-a}$$

$$C_{eq} = C_1 + C_2 = \frac{2\pi\epsilon_0 ab}{b-a} (k_1 + k_2)$$

case-VII → When dielectric slab is inserted in charged capacitor →

|a| → When battery is disconnected →

$$[Q = \text{const}]^*$$

$$C_i = \frac{A\epsilon_0}{d}$$

$$V' = V/K$$

$$C' = KC$$

$$+||-$$

iii) → capacitance (C) = KC

iii) → $E = \frac{V}{d} \Rightarrow K' = \frac{E}{K}$

iii) → potential = $\frac{V}{K}$

iv) → $W_{ext} = U' = \frac{U}{K}$

$$W_{ext} = \Delta U = \Theta ve.$$

|b| → When battery remains connected →

$$[V = \text{const}]^*$$

ii) → capacitance (C) $\Rightarrow C' = KC$

iv) → pot energy (U) $\Rightarrow U' = KU$

iii) → charge (Q) = $Q' = KQ$

v) → $W_{ext} = ?$


iii) → Electric field (E) $\Rightarrow \text{const.}$

$$W_{ext} + W_{battery} = \Delta U$$

$$W_{ext} = (K-1)\frac{CV^2}{2} - (K-1)CV^2$$

$$* W_{ext} = -\frac{1}{2}CV^2(K-1) < 0$$

NOTE →

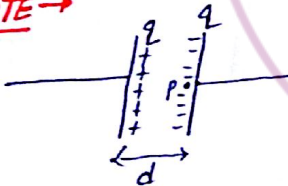

Electric field at P due to +Q plate

$$* E_p = \frac{Q}{2A\epsilon_0}$$

Force on 2nd plate $\Rightarrow F = QE_p = \frac{Q^2}{2A\epsilon_0}$

case-VIII → Force acting on dielectric slab while insertion.

|a| → When battery is disconnected - (system have only capacitor)

$$F = -\frac{dU_{capacitor}}{dx}$$

$$* U_{capacitor} = \frac{1}{2} \frac{Q^2}{C} = \frac{Q^2}{2(Ax+b)}$$

$$* F = -\frac{dU}{dx}$$

|b| → When battery remain connected →

$$dU = dU_{capacitor} + dU_{battery}$$

$$* dU_{battery} = -dW_{battery}$$

$$\checkmark \text{charge release from battery } (dq) = (dC)V$$

$$* dq = \frac{(K-1)\epsilon_0 V}{d} (dx)$$

$$F = -\frac{dU_{system}}{dx}$$

$$* F = \frac{(K-1)\epsilon_0 V^2}{2d} = \text{const.}$$