

**JEE MAIN**

---

**PREVIOUS YEAR QUESTION**

---

# **ALTERNATING CURRENT**

**PHYSICS**

---

**BY LEARNINGMANTRAS.COM**

## Alternating Current

**Q1: A series AC circuit containing an inductor (20 mH), a capacitor (120 F) and a resistor (60  $\Omega$ ) is driven by an AC source of 24 V/50 Hz. The energy dissipated in the circuit in 60 s is**

- (a)  $3.39 \times 10^3$  J
- (b)  $5.65 \times 10^2$  J
- (c)  $2.26 \times 10^3$  J
- (d)  $5.17 \times 10^2$  J

### Solution

Impedance,

$$Z = (R^2 + (X_C - X_L)^2)^{1/2}$$

$$X_L = \omega L = (2\pi\nu L)$$

$$X_L = 6.28 \times 50 \times 20 \times 10^{-3} = 6.28 \Omega$$

$$X_C = (1/\omega C) = 1/(2\pi\nu C) = 1/(6.28 \times 120 \times 10^{-6} \times 50) = 26.54 \Omega$$

$$X_C - X_L = 26.54 - 6.28 = 20.26$$

$$Z = ((60)^2 + (20.26)^2)^{1/2}$$

$$Z = 4010 \Omega$$

Average power dissipated,  $P_{av} = \epsilon_{rms} I_{rms} \cos \Phi$

$$P_{av} = \epsilon_{rms} \times (\epsilon_{rms}/Z) \times (R/Z)$$

$$P_{av} = (\epsilon_{rms}^2/Z^2) \times R = [(24)^2/4010] \times 60 \text{ W} = 8.62 \text{ W}$$

$$\text{Energy dissipated in 60 S} = 8.62 \times 60 = 5.17 \times 10^2 \text{ J}$$

**Answer: (d)  $5.17 \times 10^2$  J**

**Q2: In an AC generator, a coil with N turns, all of the same area A and total resistance R, rotates with frequency  $\omega$  in a magnetic field B. The maximum value of emf generated in the coil is**

- (a) NAB
- (b) NABR
- (c)  $NAB\omega$
- (d)  $NABRc$

**Answer: (c) In an a.c. generator, maximum emf =  $NAB\omega$**

**Q3: The phase difference between the alternating current and emf is  $\pi/2$ . Which of the following cannot be the constituent of the circuit?**

- (a) LC
- (b) L alone

(c) C alone

(d) R, L

**Solution**

R and L cause phase difference to lie between 0 and  $\pi/2$  but never 0 and  $\pi/2$  at extremities

**Answer: (d) R, L**

**Q4: Alternating current cannot be measured by D.C ammeter because**

(a) A.C cannot pass through D.C ammeter

(b) A.C changes direction

(c) The average value of current for the complete cycle is zero

(d) D.C. ammeter will get damaged

**Solution**

The average value of A.C for the complete cycle is zero. Hence A.C cannot be measured by D.C ammeter

**Answer: (c) The average value of current for the complete cycle is zero**

**Q5: A power transmission line feeds input power at 2300 V to a step-down transformer with its primary windings having 4000 turns. The output power is delivered at 230 V by the transformer. If the current in the primary of the transformer is 5 A and its efficiency is 90%, the output current would be**

(a) 25 A

(b) 50 A

(c) 45 A

(d) 35 A

**Solution**

Given  $e_p = 2300$  V,  $N_p = 4000$

$e_s = 230$  V,

$I_p = 5$  A,

$\eta = 90\% = 0.9$

$\eta = P_o/P_i = (e_s I_s)/(e_p I_p)$

$I_s = \eta e_p I_p / e_s = (0.9 \times 2300 \times 5) / 230 = 45$  A

**Answer: (c) 45 A**

**Q6: A circuit connected to an ac source of emf  $e = e_0 \sin(100 t)$  with t in seconds, gives a phase difference of  $\pi/4$  between the emf e and current I. Which of the following circuits will exhibit this?**

(a) RC circuit with  $R = 1$  k $\Omega$  and  $C = 10\mu$ F

(b) RL circuit with  $R = 1$  k $\Omega$  and  $L = 10$ mH

(c) RC circuit with  $R = 1$  k $\Omega$  and  $C = 1\mu$ F

(d) RL circuit with  $R = 1$  k $\Omega$  and  $L = 1$ mH

**Solution**

$$X_c = R$$

$$1/\omega C = R$$

$$\omega = 100 \text{ rad/s}$$

$$\text{Therefore, } 1/100 = RC$$

Substituting values from option (a)

$$R = 1 \text{ k}\Omega = 10^3 \Omega$$

$$C = 10 \mu\text{F} = 10 \times 10^{-6} \text{ F}$$

$$RC = 10^3 \times 10 \times 10^{-6} = 1/100$$

Therefore, option (a) is correct

**Answer (a) RC circuit with R = 1 kΩ and C = 10μF**

**Q7: In an a.c. circuit, the instantaneous e.m.f. and current is given by**

$$e = 100\sin 30t, i = 20\sin(30t - \pi/4)$$

**In one cycle of A.C, the average power consumed by the circuit and the wattless current are, respectively**

- (a) 50, 10
- (b)  $1000/\sqrt{2}$ , 10
- (c)  $50/\sqrt{2}$ , 0
- (d) 50, 0

**Solution**

$$P_{\text{avg}} = V_{\text{rms}} I_{\text{rms}} \cos\theta$$

$$P_{\text{avg}} = (V_0/\sqrt{2}) (I_0/\sqrt{2}) \cos\theta$$

$$= (100/\sqrt{2}) (20/\sqrt{2}) \cos 45^\circ$$

$$P_{\text{avg}} = 1000/\sqrt{2} \text{ watt}$$

$$\text{Wattless current} = I_{\text{rms}} \sin\theta$$

$$\text{Wattless current} = (I_0/\sqrt{2}) \sin\theta$$

$$= (20/\sqrt{2}) \sin 45^\circ$$

$$= 10 \text{ amp}$$

**Answer: (b)  $1000/\sqrt{2}$ , 10**

**Q8: A coil having n turns and resistance R Ω is connected with a galvanometer of resistance 4RΩ. This combination is moved in time "t" seconds from a magnetic field W<sub>1</sub> weber to W<sub>2</sub> weber. The induced current in the circuit is**

- (a)  $-(W_2 - W_1)/5Rnt$
- (b)  $-n(W_2 - W_1)/5Rt$
- (c)  $-(W_2 - W_1)/Rnt$

(d)  $-(W_2 - W_1)/5Rnt$

**Solution**

The emf induced in the coil is  $e = -n(d\Phi/dt)$

Induced current,  $I = e/R' = - (n/R')(d\Phi/dt) \text{ ---(1)}$

Given,  $R' = R + 4R = 5R$

$d\Phi = W_2 - W_1$

$dt = t$

(here,  $W_1$  and  $W_2$  are flux associated with one turn)

Substituting the given values in equa(1) we get

$I = (-n/5R)(W_2 - W_1/t)$

**Answer: (b)  $-n(W_2 - W_1)/5Rt$**

**Q9: An alternating voltage  $V(t) = 220 \sin 100\pi t$  volts is applied to a purely resistive load of  $50 \Omega$ . The time taken for the current to rise from half of the peak value is**

(a) 5 ms

(b) 2.2 ms

(c) 7.2 ms

(d) 3.3 ms

**Solution**

As  $v(t) = 220 \sin 100\pi t$

So  $I(t) = (220/50) \sin 100\pi t$

I.e.,  $I = I_m \sin 100\pi t$

For  $I = I_m$

$t_1 = (\pi/2) \times (1/100\pi) = (1/200) \text{ sec,}$

And for  $I = I_m/2$

$\Rightarrow (I_m/2) = I_m \sin(100\pi t_2)$

$\Rightarrow (\pi/6) = 100\pi t_2$

$\Rightarrow t_2 = (1/600) \text{ s}$

$\therefore t_{\text{req}} = (1/200) - (1/600) = (2/600) = (1/300) \text{ s} = 3.3 \text{ ms}$

**Answer: (d) 3.3 ms**

**Q10: An arc lamp requires a direct current of 10A at 80V to function. If it is connected to a 220V (RMS), 50 Hz AC supply, the series inductor needed for it to work is close to**

(a) 0.065 H

(b) 80 H

(c) 0.08 H

(d) 0.044 H

**Solution**

$$I = 10\text{A}$$

$$V = 80\text{ V}$$

$$R = 8\ \Omega$$

$$10 = 220 / (8^2 + X_L^2)^{1/2}$$

$$64 + X_L^2 = 484$$

$$X_L = \sqrt{420}$$

$$2\pi \times 50L = \sqrt{420}$$

$$L = \sqrt{420} / 100\pi$$

$$L = 0.065\text{ H}$$

**Answer: (a) 0.065 H**

**Q11: In a series, LCR circuit  $R = 200\ \Omega$  and the voltage and the frequency of the main supply is 220 V and 50 Hz respectively. On taking out the capacitance from the circuit the current lags behind the voltage by  $30^\circ$ . On taking out the inductor from the circuit the current leads the voltage by  $30^\circ$ . The power dissipated in the LCR circuit is**

(a) 242 W

(b) 305 W

(c) 210 W

(d) Zero

**Solution**

$$\tan \Phi = (X_L - X_C) / R$$

$$\tan 30^\circ = X_C / R = X_C = R / \sqrt{3}$$

$$\tan 30^\circ = X_L / R = X_L = R / \sqrt{3}$$

$$X_L = X_C \Rightarrow \text{Condition for resonance}$$

$$\text{So } \Phi = 0^\circ$$

$$P = VI \cos 0^\circ$$

$$P = V^2 / R = (220)^2 / 200 = 242\text{ W}$$

**Answer: (a) 242 W**

### JEE Main Chapter Wise Questions And Solutions

JEE Main Physics Previous Year Chapter Wise Questions With Solutions	<a href="#">Click Here</a>
JEE Main Chemistry Previous Year Chapter Wise Questions With Solutions	<a href="#">Click Here</a>
JEE Main Mathematics Previous Year Chapter Wise Questions With Solutions	<a href="#">Click Here</a>

### MCQ Link for NEET/JEE

JEE/NEET Physics MCQ	<a href="#">Click Here</a>
NEET/JEE Chemistry MCQ	<a href="#">Click Here</a>
NEET Biology MCQ	<a href="#">Click Here</a>
JEE Math's MCQ	<a href="#">Click Here</a>

### Notes PDF Link for NEET/JEE

Physics Notes PDF	<a href="#">Click Here</a>
Chemistry Notes PDF	<a href="#">Click Here</a>
Biology Notes PDF	<a href="#">Click Here</a>
Math's Notes PDF	<a href="#">Click Here</a>

## [Follow on Facebook](#)

By Team [Learning Mantras](#)