

JEE MAIN

PREVIOUS YEAR QUESTION

CAPACITOR

PHYSICS

BY LEARNINGMANTRAS.COM

Capacitor

Q1: A parallel plate capacitor with plates of area 1 m² each are at a separation of 0.1 m. If the electric field between the plates is 100 N C⁻¹, the magnitude of charge on each plate is

(Taken $\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{N m}^2$)

- (a) $8.85 \times 10^{-10} \text{ C}$
- (b) $7.85 \times 10^{-10} \text{ C}$
- (c) $9.85 \times 10^{-10} \text{ C}$
- (d) $6.85 \times 10^{-10} \text{ C}$

Solution

The electric field between two plates is

$$E = \sigma/\epsilon_0 = q/A\epsilon_0 \Rightarrow q = EA\epsilon_0$$


$$q = (100)(1)(8.85 \times 10^{-12}) = 8.85 \times 10^{-10} \text{ C}$$

Answer: (a) $8.85 \times 10^{-10} \text{ C}$

Q2: The parallel combination of two air filled parallel plate capacitors of capacitance C and nC is connected to a battery of voltage, V. When the capacitors are fully charged, the battery is removed and after that a dielectric material of dielectric constant K is placed between the two plates of the first capacitor. The new potential difference of the combined system is

- (a) V
- (b) $(n+1)V/(K+n)$
- (c) $(nV)/(K+n)$
- (d) $V/(K+n)$

Solution

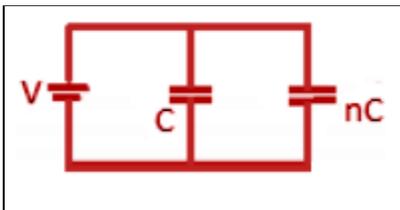

For parallel combination, $C_{eq} = C + nC = C(n + 1)$

Charge on capacitor, $q = C_{eq}V = CV(n + 1)$

Now, after removing the battery, dielectric material is placed.

Then, $C_{eq} = KC + nC = C(K + n)$

New potential difference, $V' = q/C_{eq} = CV(n+1)/C(K+n) = (n+1)V/(K+n)$

Answer: (b) $(n+1)V/(K+n)$

Q3: A parallel plate capacitor is made by stacking n equally spaced plates connected alternatively. If the capacitance between any two adjacent plates is C then the resultant capacitance is

- (a) C
- (b) nC
- (c) $(n - 1)C$
- (d) $(n + 1)C$

Solution

n plates connected alternately give rise to $(n - 1)$ capacitors connected in parallel

Resultant capacitance = $(n - 1)C$.

Answer: (c) $(n - 1)C$

Q4: Capacitance (in F) of a spherical conductor with radius 1 m is

- (a) 1.1×10^{-10}
- (b) 10^{-6}
- (c) 9×10^{-9}
- (d) 10^{-3}

Solution

$C = 4\pi\epsilon_0 R = 1/9 \times 10^9 = 1.1 \times 10^{-10}$ F

Answer: (a) 1.1×10^{-10}

Q5: If there are n capacitors in parallel connected to V volt source, then the energy stored is equal to

- (a) CV
- (b) $(\frac{1}{2})nCV^2$
- (c) CV^2
- (d) $(1/2n)CV^2$

Solution


Total capacity = nC

\therefore Energy = $\frac{1}{2} nCV^2$

Answer: (b) $(\frac{1}{2})nCV^2$

Q6: A parallel plate capacitor with air between the plates has a capacitance of 9 pF. The separation between its plates is d . The space between the plates is now filled with two dielectrics. One of the dielectrics has dielectric constant $k_1 = 3$ and thickness $d/3$ while the other one has dielectric constant $k_2 = 6$ and thickness $2d/3$. The capacitance of the capacitor is now

- (a) 20.25 pF
- (b) 1.8 pF
- (c) 45 pF
- (d) 40.5 pF

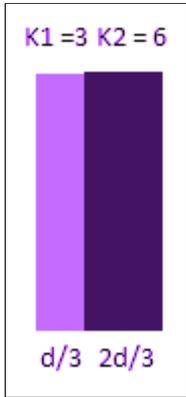Solution

$$C = \epsilon_0 A / d = 9 \times 10^{-12} \text{ F}$$

With dielectric, $C = \epsilon_0 A k / d$

$$C_1 = \epsilon_0 A 3 / (d/3) = 9C$$

$$C_2 = \epsilon_0 A 6 / (2d/3) = 9C$$

$C_{\text{total}} = C_1 C_2 / (C_1 + C_2)$ as they are in series

$$C_{\text{total}} = (9C \times 9C) / 18C = (9/2)C = (9/2)(9 \times 10^{-12} \text{ F})$$

$$C_{\text{total}} = 40.5 \text{ pF}$$

Answer: (d) 40.5 pF

Q7: A parallel plate condenser with a dielectric constant K between the plates has a capacity C and is charged to a potential V volt. The dielectric slab is slowly removed from between the plates and then reinserted. The net work done by the system in this process is

- (a) zero
- (b) $1/2 (K - 1) CV^2$
- (c) $CV^2(K-1)/K$
- (d) $(K - 1) CV^2$

Solution

The potential energy of a charged capacitor

$$U_i = q^2 / 2C$$

where U_i is the initial potential energy.

If a dielectric slab is slowly introduced, the energy = $q^2 / 2KC$

Once it is taken out, again the energy increases to the old value. Therefore after it is taken out, the potential energy comes back to the old value.

Total work done = zero.

Answer: (a) zero

Q8: A battery is used to charge a parallel plate capacitor till the potential difference between the plates becomes equal to the electromotive force of the battery. The ratio of the energy stored in the capacitor and the work done by the battery will be

- (a) 1/2
- (b) 1
- (c) 2
- (d) 1/4

Solution

Let E be emf of the battery

Work done by the battery $W = CE^2$

Energy stored in the capacitor

$$U = \frac{1}{2}CE^2$$

$$U/W = \frac{1}{2}CE^2 / CE^2 = \frac{1}{2}$$

Answer: (a) 1/2

Q9: A sheet of aluminium foil of negligible thickness is introduced between the plates of a capacitor. The capacitance of the capacitor

- (a) decreases
- (b) remains unchanged
- (c) becomes infinite
- (d) increases

Solution

Aluminium is a good conductor. Its sheet introduced between the plates of a capacitor is of negligible thickness. Therefore, capacity remains unchanged.

With air as dielectric, $C = \epsilon_0 A/d$

With space partially filled, $C' = \epsilon_0 A/(d-t) = \epsilon_0 A/d = C$

Answer: (b) remains unchanged

Q10: If the electric flux entering and leaving an enclosed surface respectively is Φ_1 and Φ_2 , the electric charge inside the surface will be

- (a) $(\Phi_2 - \Phi_1)\epsilon_0$
- (b) $(\Phi_1 + \Phi_2)/\epsilon_0$
- (c) $(\Phi_2 - \Phi_1)/\epsilon_0$
- (d) $(\Phi_1 + \Phi_2)\epsilon_0$

Solution

According to Gauss theorem,

$$(\Phi_2 - \Phi_1) = Q/\epsilon_0$$

$$\Rightarrow Q = (\Phi_2 - \Phi_1)\epsilon_0$$

The flux enters the enclosure if one has a negative charge ($-q_2$) and flux goes out if one has a +ve charge ($+q_1$). As one does not know whether $\Phi_1 > \Phi_2$, $\Phi_2 > \Phi_1$, $Q = q_1 \sim q_2$

Answer: (a) $(\Phi_2 - \Phi_1)\epsilon_0$

Q11: A parallel plate capacitor is of area 6 cm² and a separation of 3 mm. The gap is filled with three dielectric materials of equal thickness (see figure) with dielectric constants $K_1 = 10$, $K_2 = 12$ and $K_3 = 14$. The dielectric constant of a material which when fully inserted in the given capacitor gives the same capacitance would be



- (a) 36
- (b) 12
- (c) 4
- (d) 14

Solution

The given system can be considered to be a parallel combination of three capacitors C_1 , C_2 and C_3 . The equivalent capacitance, $C = C_1 + C_2 + C_3$

$$\text{Hence, } C_1 = K_1\epsilon_0A/3d$$

$$C_2 = K_2\epsilon_0A/3d$$


$$C_3 = K_3\epsilon_0A/3d$$

$$(K'\epsilon_0A/d) = (K_1 + K_2 + K_3/3)(\epsilon_0A/d)$$

$$\text{Hence } K' = (K_1 + K_2 + K_3/3) = (10 + 12 + 14/3) = 12$$

Answer: (b) 12

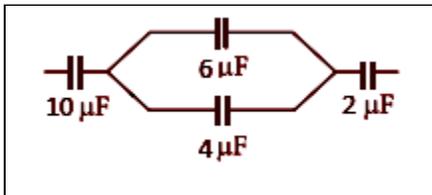Q12: In the figure shown below, the charge on the left plate of the 10 F capacitor is -30 C. The charge on the right plate of the 6 F capacitor is



- (a) $-18 \mu\text{C}$
- (b) $-12 \mu\text{C}$
- (c) $+12 \mu\text{C}$
- (d) $+18 \mu\text{C}$

Solution

Let q_1 and q_2 be the charge on $6\mu\text{F}$ and $4\mu\text{F}$ respectively

$$q_1 + q_2 = q \text{---(1)}$$

$$\text{Also, } (q_1/C_1) = (q_2/C_2) \text{---(2)}$$

(\because C_1 and C_2 are in parallel combination)


$$\Rightarrow q_2 = (C_2/C_1) q_1 = (4/6)q_1$$

Using (1) and (2)

$$(10/6)q_1 = q \Rightarrow q = (5/3)q_1 \Rightarrow (\frac{3}{5})(30) = 18 \mu\text{C}$$

Answer: (d) $+18 \mu\text{C}$

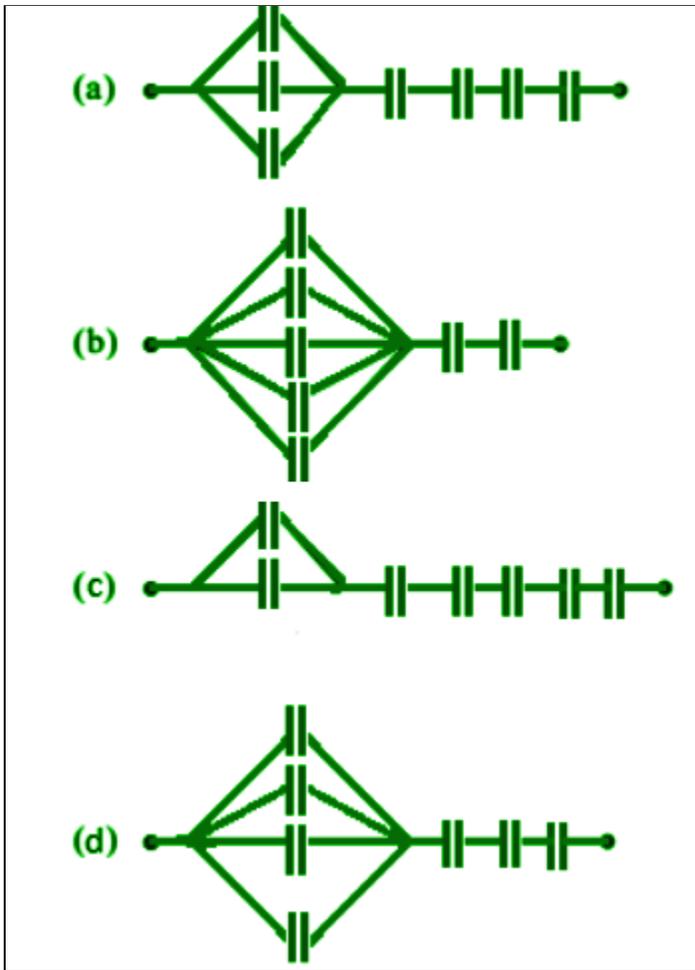Q13: Seven capacitors, each of capacitance 2 F, are to be connected in a configuration to obtain an effective capacitance of $(6/13)$ F. Which of the combinations, shown in figures below, will achieve the desired value?



Solution

Equivalent capacitance for parallel capacitors is given by the formula

$$C_{eq} = C_1 + C_2 + C_3 \dots$$

$$\text{Therefore, } 1/C_{eq} = 1/(C_1 + C_2 + C_3)$$

Equivalent capacitance for series capacitors is given by the formula

$$1/C_{eq} = 1/C_1 + 1/C_2 + 1/C_3$$

In option "a" there are 3 parallel capacitors and 4 series capacitors

Therefore, Equivalent capacitance = $1/(2+2+2) + (1/2) + (1/2) + (1/2) + (1/2)$

$$= 1/6 + (1/2) + (1/2) + (1/2) + (1/2)$$

$$= 1+3+3+3+3/6$$

$$1/C_{eq} = 13/6 \text{ F}$$

$$C_{eq} = (6/13) \text{ F}$$

In option "b" there are 5 parallel capacitors and 2 series capacitors

Therefore, Equivalent capacitance = $1/(2+2+2+2+2) + (1/2) + (1/2)$

$$= 1/10 + (1/2) + (1/2)$$

$$= 1+5+5/10$$

$$1/C_{eq} = 11/10 \text{ F}$$

$$C_{eq} = 10/11 \text{ F}$$

In option "c" there are 2 parallel capacitors and 5 series capacitors

Therefore, Equivalent capacitance = $1/(2+2) + (1/2) + (1/2) + (1/2) + (1/2) + (1/2)$

$$= 1/4 + (1/2) + (1/2) + (1/2) + (1/2) + (1/2)$$

$$= 1+2+2+2+2+2/4$$

$$1/C_{eq} = 11/4 \text{ F}$$

$$C_{eq} = (4/11) \text{ F}$$

In option "d" there are 4 parallel capacitors and 3 series capacitors

Therefore, Equivalent capacitance = $1/(2+2+2+2) + (1/2) + (1/2) + (1/2)$


$$= 1/8 + (1/2) + (1/2) + (1/2)$$

$$= 1+4+4+4/4$$

$$1/C_{eq} = 13/8 \text{ F}$$

$$C_{eq} = (8/13) \text{ F}$$

Answer (a)

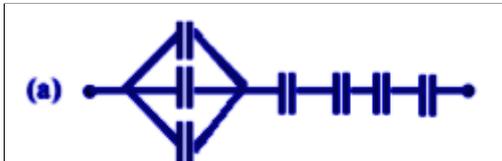

Q14: Voltage rating of a parallel plate capacitor is 500 V. Its dielectric can withstand a maximum electric field of 10^6 V m^{-1} . The plate area is 10^{-4} m^2 . What is the dielectric constant if the capacitance is 15 pF? (given $\epsilon_0 = 8.86 \times 10^{-12} \text{ C}^2 \text{ N}^{-1} \text{ m}^{-2}$)

- (a) 3.8
- (b) 8.5
- (c) 6.2
- (d) 4.5

Solution

$$C = K\epsilon_0 A/d \text{ or } K = CV/\epsilon_0 A E_{\max}$$

$$K = (15 \times 10^{-12} \times 500)/(8.86 \times 10^{-12} \times 10^{-4} \times 10^6) = 8.5$$

Answer: (b) 8.5

Q15: In free space, a particle A of charge 1 C is held fixed at a point P. Another particle B of the same charge and mass 4 g is kept at a distance of 1 mm from P. If B is released, then its velocity at a distance of 9 mm from P is

(take $1/4\pi\epsilon_0 = 9 \times 10^9 \text{ Nm}^2\text{C}^{-2}$)

- (a) $3.0 \times 10^4 \text{ m/s}$
- (b) 1.0 m/s
- (c) $1.5 \times 10^2 \text{ m/s}$
- (d) $2.0 \times 10^3 \text{ m/s}$

Solution

Using work energy theorem

$$W_E = U_i - U_f = \frac{1}{2}mv^2 \text{ or } kq_1q_2\left[\frac{1}{r_1} - \frac{1}{r_2}\right] = \frac{1}{2}mv^2$$

$$W_E = (9 \times 10^9) \times (1 \times 10^{-6})^2 \left\{ \frac{1}{10^{-3}} - \frac{1}{(9 \times 10^{-3})} \right\} = \frac{1}{2}mv^2$$

$$\Rightarrow (9 \times 10^9 \times 2 \times 10^{-12}) / (4 \times 10^{-6}) = v^2 \Rightarrow v = 2.0 \times 10^3 \text{ ms}^{-1}$$

Answer: (d) $2.0 \times 10^3 \text{ m/s}$

JEE Main Chapter Wise Questions And Solutions

| | |
|--|----------------------------|
| JEE Main Physics Previous Year Chapter Wise Questions With Solutions | Click Here |
| JEE Main Chemistry Previous Year Chapter Wise Questions With Solutions | Click Here |
| JEE Main Mathematics Previous Year Chapter Wise Questions With Solutions | Click Here |

MCQ Link for NEET/JEE

| | |
|------------------------|----------------------------|
| JEE/NEET Physics MCQ | Click Here |
| NEET/JEE Chemistry MCQ | Click Here |
| NEET Biology MCQ | Click Here |
| JEE Math's MCQ | Click Here |

Notes PDF Link for NEET/JEE

| | |
|---------------------|----------------------------|
| Physics Notes PDF | Click Here |
| Chemistry Notes PDF | Click Here |
| Biology Notes PDF | Click Here |
| Math's Notes PDF | Click Here |

[Follow on Facebook](#)

By Team [Learning Mantras](#)